

14 Sin режим в RLC-двууполосник...

Закона на Ом в комплексен вид

$$R_i + L \frac{di}{dt} + \frac{1}{C} \int idt = u(t)$$

$$u(t) = u_m \sin(\omega t + \psi_u)$$

Търсим стационарния ток:

$$i(t) = i_m \sin(\omega t + \psi_i) = \sqrt{2} I \sin(\omega t + \psi_i)$$

$$\sum U_k = \sum e_k$$

$$U_R + U_L + U_C - u = 0$$

$$R_i + L \frac{di}{dt} + \frac{1}{C} \int idt = 0$$

Метод на комплексната амплитуда:

$$K \left[R_i + L \frac{di}{dt} + \frac{1}{C} \int idt \right] = K [u(t)]$$

$$K [R_i] + K \left[L \frac{di}{dt} \right] + K \left[\frac{1}{C} \int idt \right] = \dot{u}(t)$$

$$K [u(t)] = \dot{u}(t) = u_m e^{j(\omega t + \psi_u)} = \sqrt{2} U e^{j(\omega t + \psi_u)}$$

$$R \dot{i}(t) + L \frac{d^2 i}{dt^2} + \frac{1}{C} \int i dt = \dot{u}(t)$$

$$i(t) = I_m [i(t)]; \quad u(t) = I_m [\dot{u}(t)]$$

$$R \dot{i}(t) + j\omega L i(t) + \frac{1}{j\omega C} i(t) = \dot{u}(t)$$

$$R + j\omega L + \frac{1}{j\omega C} \int i(t) dt = \dot{u}(t)$$

$$\frac{1}{j\omega C} = -j \frac{1}{\omega C}$$

$$i(t) = \sqrt{2} \dot{i} e^{j\omega t}; \quad u(t) = \sqrt{2} \dot{u} e^{j\omega t}$$

$$\dot{U} = U e^{j\psi_u}$$

$$\left[R + j\left(\omega L - \frac{1}{\omega C}\right) \right] \sqrt{2} \dot{i} e^{j\omega t} = \sqrt{2} \dot{u} e^{j\omega t}$$


$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \quad \dot{U} = Z \dot{I}$$

Комплексен импеданс ≡ компл. съпротив.

Символически метод (м. ч/з компл. образи)

$$\dot{I} \frac{\dot{U}}{Z}, \quad \dot{I} \rightarrow i(t)$$
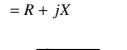
$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) = R + j(X_L - X_C) = R + jX$$



$$X_L = \omega L - \text{индуктивно}$$

$$X_C = \frac{1}{\omega C} - \text{капацитивно}$$

$$X = X_L - X_C = \omega L - \frac{1}{\omega C} - \text{реактивно}$$

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) = R + jX =$$

$$= \sqrt{R^2 + X^2} e^{j \arctg \frac{X}{R}} = z e^{j\varphi}$$

$$\underline{Z} = z e^{j\varphi}$$

$$Z = z e^{j\varphi} = z \cos \varphi + j z \sin \varphi = R + jX$$

$$z = \text{mod } Z$$

$$R = z \cos \varphi - \text{реална част на } Z = \text{Re}\{Z\}$$

$$X = z \sin \varphi = I_m [Z]$$

$$z = \sqrt{R^2 + X^2}$$

Комплексен вид на закона на Ом

$$\dot{U} = Z \dot{I}, \quad Z = z e^{j\varphi}$$

$$\dot{U} = U e^{j\psi_u}, \quad U e^{j\psi_u} = z I e^{j(\psi_i + \varphi)}$$

$$\dot{I} = I e^{j\psi_i} \quad |U = z I \quad \psi_u = \psi_i + \varphi$$

$$\varphi = \psi_u - \psi_i = \arctg \frac{X}{R}$$


Елемент	Компл. импеданс
R	$Z_R = R$
L	$Z_L = j\omega L = jX_L$
C	$Z_C = -\frac{1}{j\omega C} = -jX_C$

Векторна диаграма с компл. величина.

$$M = a + jb = r e^{j\psi}$$

$$j = e^{j\frac{\pi}{2}}, \quad M = r e^{j\psi}$$
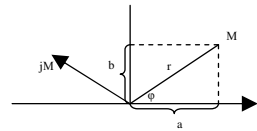
$$jM = e^{j\frac{\pi}{2}} r e^{j\psi} = r e^{j(\psi + \frac{\pi}{2})}$$



Умнож. по j е завъртане на 90 в права пос.

$$\dot{U} = Z \dot{I}$$

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) = R + j\omega - j \frac{1}{\omega C}$$

$$\dot{U} = R \dot{I} + j\omega L \dot{I} - j \frac{1}{\omega C} \dot{I}$$

$$\dot{U}_R = R \dot{I}$$

$$\dot{U}_L = j\omega L \dot{I} \quad \dot{U} = \dot{U}_R + \dot{U}_L + \dot{U}_C$$

$$\dot{U}_C = -j \frac{1}{\omega C} \dot{I}$$