

47 Взаимни връзки м/у пасивните елементи в 4П

1.  $[Z]=[Y]^{-1}$

$$[Y]=[Z]^{-1}$$

2.

$$[A],[Y]$$

$$[A]=\begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$[Y]=\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

$$[A]=\begin{bmatrix} \frac{Y_{22}}{Y_{21}} & \frac{1}{Y_{21}} \\ \frac{Y_{11}Y_{22}-Y_{12}Y_{21}}{Y_{21}} & \frac{Y_{11}}{Y_{21}} \end{bmatrix}$$

У параметри чрез А

$$\dot{U}_1 = A\dot{U}_2 + B\dot{I}_2$$

$$\dot{I}_1 = C\dot{U}_2 + D\dot{I}_2$$

$$\dot{I}_1 = \frac{1}{R}\dot{U}_1 - \frac{A}{B}\dot{U}_2$$

$$\dot{I}_1 = C\dot{U}_2 + D\left(\frac{1}{B}\dot{U}_1 - \frac{A}{B}\dot{U}_2\right)$$

$$\dot{I}_1 = C\dot{U}_2 + \frac{D}{B}\dot{U}_1 - \frac{AD}{B}\dot{U}_2$$

$$\dot{I}_1 = \frac{D}{B}\dot{U}_1 - \frac{AD-BC}{B}\dot{U}_2 = Y_{11}\dot{U}_1 - Y_{12}\dot{U}_2$$

$$\dot{I}_2 = \frac{1}{B}\dot{U}_1 - \frac{A}{B}\dot{U}_2 = Y_{21}\dot{U}_1 - Y_{22}\dot{U}_2$$

$$[Y]=\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} =$$

$$\begin{bmatrix} \frac{D}{B} & \frac{AD-BC}{B} \\ \frac{1}{B} & \frac{A}{B} \end{bmatrix}$$

за взаимен 4П

$$AD-BC=1$$

$$[Y]=\begin{bmatrix} \frac{D}{B} & \frac{1}{B} \\ \frac{1}{B} & \frac{A}{B} \end{bmatrix}$$