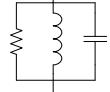


### 36. Токов резонанс в GLC двуполюсник



$$Y = G - j\left(\frac{1}{\omega L} - \omega C\right) = G - jB;$$

$$y = \sqrt{G^2 + \left(\frac{1}{\omega L} - \omega C\right)^2}; \text{Im}[Y_p] = B_p = 0;$$

$$B = \frac{1}{\omega L} - \omega C; \quad B_p = \frac{1}{\omega_p L} - \omega_p C;$$

$$\omega_p = \frac{1}{\sqrt{LC}}; \quad Y_p = y_p = G - \text{минимум}$$

$$\gamma = \sqrt{\frac{C}{L}}; [\gamma] = s;$$

$$B_{Lp} = \frac{1}{\omega_p L} = \frac{\sqrt{LC}}{L} = \sqrt{\frac{C}{L}} = \gamma;$$


$$B_{Cp} = \omega_p C = \frac{C}{\sqrt{LC}} = \sqrt{\frac{C}{L}} = \gamma \Rightarrow B_L$$

$$p = B_{Cp} = \gamma; \quad I = yU; \quad U = I/y; \quad \Rightarrow U_p = \frac{I}{G};$$

$$>\max. \quad I_{Lp} = B_{Lp}U_p = \gamma \frac{I}{G} = \frac{\gamma}{G} I;$$

$$I_{Cp} = B_{Cp}U_p = \gamma \frac{I}{G} = \frac{\gamma}{G} I$$
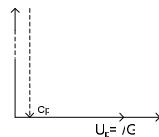
$$Q = \frac{\gamma}{G} \cdot \text{качествен фактор}$$



$$U = u_m \sin(\omega t + \varphi_u);$$

$$i_L = \frac{1}{L} \int u dt = -\frac{1}{\omega L} u_m \cos(\omega t + \varphi_u)$$

Енергия:

$$W = W_C + W_L = \frac{1}{2} CU^2 + \frac{1}{2} Li^2 =$$

$$\frac{1}{2} CU_m^2 \sin^2(\omega t + \varphi_u) + \frac{1}{2} L \frac{U_m^2}{\omega^2 L^2} \cos^2(\omega t + \varphi_u)$$

$$\omega_p = \frac{1}{\sqrt{LC}}$$

$$W_p = \frac{1}{2} CU_m^2 \sin^2(\omega t + \varphi_u) + \dots$$

$$\frac{1}{2} L \frac{U_m^2}{\frac{1}{\omega_p^2} L^2} \cos^2(\omega t + \varphi_u)$$

$$W_p = \frac{1}{2} CU_m^2 (\sin^2(\omega t + \varphi_u) + \dots)$$

$$+ \cos^2(\omega t + \varphi_u)) = \frac{1}{2} CU_m^2$$

Честотни зависимости:

$$B_L(\omega) = \frac{1}{\omega L}; \quad B_C(\omega) = \omega C;$$

$$B(\omega) = \frac{1}{\omega L} - \omega C;$$

$$y(\omega) = \sqrt{G^2 + \left(\frac{1}{\omega L} - \omega C\right)^2};$$

$$\varphi(\omega) = \arctg \frac{\frac{1}{\omega L} - \omega C}{G}$$

