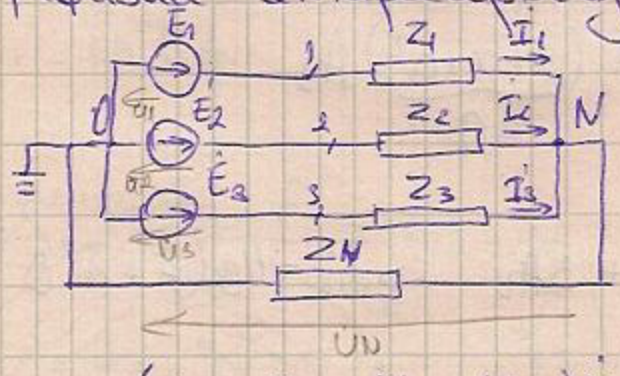


Задача №43. Измерение на нейтраль при статическом токе

1) Трехфазная четырехпроводная линия



уже применим метода с возобител потенциал

$$V_0 = 0$$

$$(Y_1 + Y_2 + Y_3 + Y_N) \dot{V}_N = Y_1 \dot{E}_1 + Y_2 \dot{E}_2 + Y_3 \dot{E}_3$$

$$\dot{V}_N = \dot{U}_{N0} = \dot{U}_N = \frac{Y_1 \dot{E}_1 + Y_2 \dot{E}_2 + Y_3 \dot{E}_3}{Y_1 + Y_2 + Y_3 + Y_N}$$

$$\dot{U}_i = \dot{E}_i, \quad i = 1, 2, 3$$

$$\dot{U}_N = \frac{Y_1 \dot{U}_1 + Y_2 \dot{U}_2 + Y_3 \dot{U}_3}{Y_1 + Y_2 + Y_3 + Y_N}$$

$$Z_1 \dot{I}_1 = \dot{E}_1 - \dot{U}_N$$

$$\dot{I}_1 = 1/Z_1 (\dot{E}_1 - \dot{U}_N) = Y_1 (\dot{E}_1 - \dot{U}_N) = Y_1 (\dot{U}_1 - \dot{U}_N)$$


$$\dot{I}_2 = Y_2 (\dot{E}_2 - \dot{U}_N) = Y_2 (\dot{U}_2 - \dot{U}_N)$$

$$\dot{I}_3 = Y_3 (\dot{E}_3 - \dot{U}_N) = Y_3 (\dot{U}_3 - \dot{U}_N)$$

$$\dot{I}_N = Y_N \dot{U}_N$$

$$\dot{I}_N = \dot{I}_1 + \dot{I}_2 + \dot{I}_3$$

2) Трехфазная трехпроводная линия

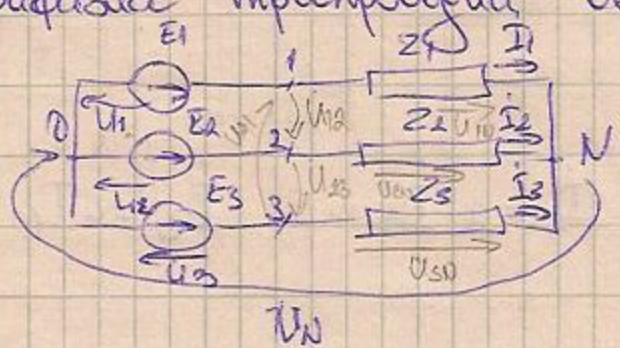

$$\dot{U}_N = \frac{Y_1 \dot{U}_1 + Y_2 \dot{U}_2 + Y_3 \dot{U}_3}{Y_1 + Y_2 + Y_3}$$

$$\dot{U}_N + \dot{U}_N - \dot{U}_1 = 0$$

$$\dot{U}_N = \dot{U}_1 - \dot{U}_N = \dot{U}_1 - \frac{Y_1 \dot{U}_1 + Y_2 \dot{U}_2 + Y_3 \dot{U}_3}{Y_1 + Y_2 + Y_3}$$

$$\dot{U}_N = \frac{Y_2 (\dot{U}_1 - \dot{U}_2) + Y_3 (\dot{U}_1 - \dot{U}_3)}{Y_1 + Y_2 + Y_3}$$

$$\dot{U}_{N1} = \frac{Y_2 \dot{U}_{12} - Y_3 \dot{U}_{31}}{Y_1 + Y_2 + Y_3}$$

$$\dot{U}_1 - \dot{U}_2 - \dot{U}_{12} = 0$$

$$\dot{U}_{12} = \dot{U}_1 - \dot{U}_2$$

$$\dot{U}_{31} = \dot{U}_3 - \dot{U}_1$$

аналогично за 2 фаза и 3 фаза

$$\dot{U}_{20} = \frac{Y_3 \dot{U}_{23} - Y_1 \dot{U}_{12}}{Y_1 + Y_2 + Y_3}$$

$$\dot{U}_{30} = \frac{Y_1 \dot{U}_{31} - Y_2 \dot{U}_{23}}{Y_1 + Y_2 + Y_3}$$

$$\dot{I}_1 = Y_1 \dot{U}_{10}$$

$$\dot{I}_2 = Y_2 \dot{U}_{20}$$

$$\dot{I}_3 = Y_3 \dot{U}_{30} \quad (\dot{I}_3 = -\dot{I}_1 - \dot{I}_2)$$

$$\dot{U}_{12} + \dot{U}_{23} + \dot{U}_{31} = 0$$