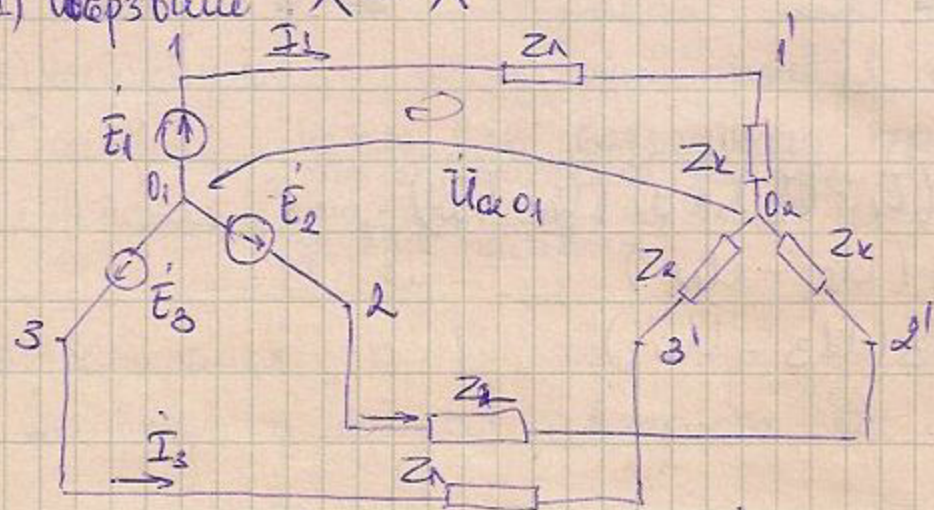


Вопрос №42 Изменение на ТСВ и

1) Преобразование $\lambda - \lambda$




$$\begin{cases} \dot{E}_1 = Z_n \cdot \dot{I}_1 + Z_k \cdot \dot{I}_1 + \dot{U}_{0201} \\ \dot{E}_2 = Z_n \cdot \dot{I}_2 + Z_k \cdot \dot{I}_2 + \dot{U}_{0201} \\ \dot{E}_3 = Z_n \cdot \dot{I}_3 + Z_k \cdot \dot{I}_3 + \dot{U}_{0201} \\ \dot{E}_1 = \dot{E}_1 \\ \dot{E}_2 = a^2 \dot{E}_1 \\ \dot{E}_3 = a \dot{E}_1 \end{cases} \quad \begin{cases} \dot{I}_1 = \dot{I}_1 \\ \dot{I}_2 = a^2 \dot{I}_1 \\ \dot{I}_3 = a \dot{I}_1 \end{cases}$$

$$(1+a+a^2)\dot{E}_1 = (1+a+a^2)Z_n \cdot \dot{I}_1 + (1+a+a^2)Z_k \cdot \dot{I}_1 + 3\dot{U}_{0201}$$

$$\Rightarrow \dot{U}_{0201} = 0$$

замещенная схема на I^{ва} фазе

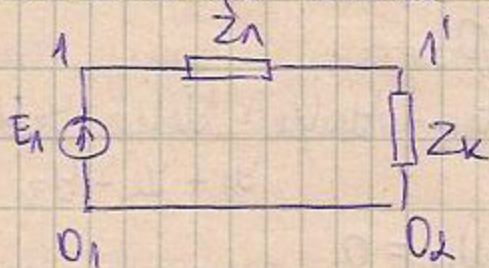

$$\dot{I}_1 = \frac{\dot{E}_1}{Z_n + Z_k}$$

$$\dot{I}_2 = a^2 \dot{I}_1$$

$$\dot{I}_3 = a \dot{I}_1$$

2) $\lambda \rightarrow \Delta$
 $\Delta \rightarrow \lambda$

